



Name:

Date:

Grade:

Worksheet about 'Electric Circuit'

Q1) Choose the correct answer.

1. A material that let's electricity pass through it is called

- a) An electrical Insulator
- b) An electrical Conductor
- c) None of them

2. A material that doesn't allow electricity to pass through it is called

.....

- a) An electrical Conductor
- b) An electrical Insulator
- c) None of them

3. Which of the following materials is an example of electrical Conductor?

- a) Silver
- b) Plastic
- c) Wood


4. Which of the following materials is an example of electrical Insulator?

- a) Gold
- b) Rubber




c) Copper

5. This circuit is

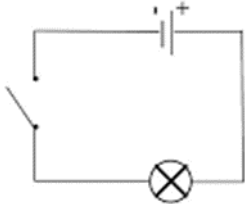

- a) Open circuit
- b) Closed circuit

6. This circuit is

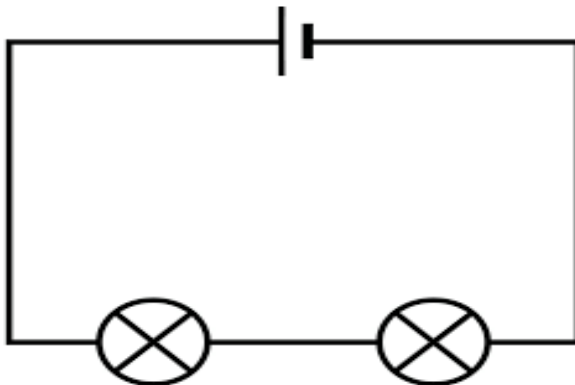

- a) Open circuit
- b) Closed circuit

7. When the circuit is closed, the switch is

- a) On
- b) Off

8. Currents flow from which side of the battery...

- a) Negative
- b) Positive
- c) I have no clue



9. What supplies energy in an electric circuit

- a) Light bulb
- b) Battery
- c) Wire

Q2) Complete the table



SYMBOL	Can you name the symbol?

	----- (-----)
	----- (-----)